

# Forms and simplifications of Boolean Expressions

# Canonical forms of a boolean expression

Standard ways of uniquely representing boolean expressions

1. Sum of *minterms*
2. Product of *maxterms*

# Terminology

# Truth table for a 3-variable logic function $F(X,Y,Z)$

Row	X	Y	Z	F
0	0	0	0	$F(0,0,0)$
1	0	0	1	$F(0,0,1)$
2	0	1	0	$F(0,1,0)$
3	0	1	1	$F(0,1,1)$
4	1	0	0	$F(1,0,0)$
5	1	0	1	$F(1,0,1)$
6	1	1	0	$F(1,1,0)$
7	1	1	1	$F(1,1,1)$

Table 1.

# Terminology (1)

Literal	A variable (X) or a complement of a variable (X')
Product term	A single literal (X) or a logical product of two or more literals (X.Y.Z)
Sum-of-products expression	A logical sum of product terms: $X + Y.Z + X'.Z$
Sum term	A single literal or a logical sum of two or more literals: $X + Y' + Z$
Product-of-sums expression	A logical product of sum terms: $Z'.(X+Y).(Y'+Z)$
Normal term	A product or sum term where no variable appears more than once: $X.Y.Z'$ , $X + Y' + Z'$ etc
Minterm	An n-variable minterm is a normal product term with n literals
Maxterm	An n-variable maxterm is a normal sum term with n literals

# Minterms and maxterms

Row	X	Y	Z	F	Minterm		Maxterm	
0	0	0	0	F(0,0,0)	$m_0$	$X'.Y'.Z'$	$M_0$	$X+Y+Z$
1	0	0	1	F(0,0,1)	$m_1$	$X'.Y'.Z$	$M_1$	$X+Y+Z'$
2	0	1	0	F(0,1,0)	$m_2$	$X'.Y.Z'$	$M_2$	$X+Y'+Z$
3	0	1	1	F(0,1,1)	$m_3$	$X'.Y.Z$	$M_3$	$X+Y'+Z'$
4	1	0	0	F(1,0,0)	$m_4$	$X.Y'.Z'$	$M_4$	$X'+Y+Z$
5	1	0	1	F(1,0,1)	$m_5$	$X.Y'.Z$	$M_5$	$X'+Y+Z'$
6	1	1	0	F(1,1,0)	$m_6$	$X.Y.Z'$	$M_6$	$X'+Y'+Z$
7	1	1	1	F(1,1,1)	$m_7$	$X.Y.Z$	$M_7$	$X'+Y'+Z'$

Table 2.

# Terminology (2)

Minterm number	An n-variable minterm can be represented by an n-bit integer
Minterm i	Minterm corresponding to the row i of the truth table
Maxterm i	Maxterm corresponding to the row i of the truth table
Canonical sum	Sum of the minterms corresponding to the truth table rows for which the output is 1. $\Sigma_{X,Y,Z} m(0,3,4,6,7) = X'.Y'.Z' + X'.Y.Z + X.Y'.Z' + X.Y.Z' + X.Y.Z$
Minterm list	$\Sigma_{X,Y,Z} m(0,3,4,6,7)$
on-set	Same as the minterm list
Canonical product	Product of maxterms corresponding to the truth table rows for which the output is 0. $\Pi_{X,Y,Z} M(1,2,5) = (X+Y+Z').(X+Y'+Z).(X'+Y+Z')$
Maxterm list	$\Pi_{X,Y,Z} M(1,2,5)$
off-set	Same as the maxterm list

# Equivalent ways of representing a combinational logic function

- Truth table
- Canonical sum of product terms
  - Algebraic sum of minterms
- Minterm list
- Canonical product of sum terms
  - Algebraic product of maxterms
- Maxterm list



# Standard Form

- This is a simplified canonical form
- Canonical form is a special case of the standard form

There are two types:

1. Sum of Products (SoP)
  - a. Products do not necessarily have to be minterms
2. Product of Sums (PoS)
  - a. Sums do not necessarily have to be maxterms

Standardization makes the evaluation, simplification, and implementation of Boolean expressions more systematic and easier.

# Sum of Products

$$X + X.Y' + X'.Y.Z$$

- Each term can contain a single literal or a logical product of multiple literals
- Can only contain complements of single variables

## **Canonical sum of products (sum of minterms)**

Each term in SoP should contain all the variables

- $ABC + A'BC' + ABC'$

# Converting a SoP into a canonical sum of minterms

**SoP (non-canonical):**  $AB + ABC + CB$

**Canonical sum of minterms:**

$$AB.(C+C') + ABC + (A+A')CB$$

$$= ABC + ABC' + ABC + ACB + A'CB$$

Since  $X + X = X$

$$\underline{ABC} + ABC' + \underline{ABC} + \underline{ACB} + A'CB$$

$$\mathbf{ABC + ABC' + A'CB}$$

# Converting a SoP into a canonical sum of minterms

**SoP (non-canonical):**  $AB + B'$

**Canonical sum of minterms:**

$$= AB + (A+A')B'$$

$$= AB + AB' + A'B'$$

$$= m_3 + m_2 + m_0$$

$$= \sum (m_3, m_2, m_0)$$

$$= \sum m(0,2,3)$$

A	B	Minterm		Maxterm	
0	0	$m_0$	$A'B'$	$M_0$	$A+B$
0	1	$m_1$	$A'B$	$M_1$	$A+B'$
1	0	$m_2$	$AB'$	$M_2$	$A'+B$
1	1	$m_3$	$AB$	$M_3$	$A'+B'$

# Product of Sums

**PoS:**  $(A+B).(A'+B+C').B$

- Product of sum terms
- Each sum term can contain a single literal or any sum of those

## **Canonical product of sums (sum of maxterms)**

- Each sum term should contain each of the variables or their complement
  - $(A+B+C')(A'+B'+C')$

# Converting a PoS into a canonical product of maxterms

**PoS:**  $(A+B).A$

**Canonical PoS:**

Use  $A = A+0$  and  $B.B'=0$

$$(A+B). (A+0)$$

$$= (A+B).(A+B.B')$$

$$= (A+B).(A+B).(A+B')$$

$$=(A+B).(A+B')$$

$$= M_0.M_1$$

$$= \prod (M_0, M_1)$$

$$= \prod M(0,1)$$

A	B	Minterm		Maxterm	
0	0	$m_0$	$A'B'$	$M_0$	$A+B$
0	1	$m_1$	$A'B$	$M_1$	$A+B'$
1	0	$m_2$	$AB'$	$M_2$	$A'+B$
1	1	$m_3$	$AB$	$M_3$	$A'+B'$

# Duality of canonical forms

- The following are equivalent:
  - $\Sigma_{X,Y,Z}m(0,3,4,6,7) = X'.Y'.Z' + X'.Y.Z + X.Y'.Z' + X.Y.Z' + X.Y.Z$
  - $\Pi_{X,Y,Z}M(1,2,5) = (X+Y+Z').(X+Y'+Z).(X'+Y+Z')$
  - A function expressed as an SoP can also be expressed as a PoS
- $\Sigma_{X,Y,Z}m(0,3,4,6,7) = \Pi_{X,Y,Z}M(1,2,5)$
- In general,  $\Sigma m(\{a\}) = \Pi M(\{b\})$  where,
  - $\{a\} \cup \{b\} = \{0,1,2,\dots,2^n-1\}$
  - $\{a\} \cap \{b\} = \{\phi\}$

# Canonical forms and De Morgan's law

A sum of minterms equals the inverse of the product of the corresponding maxterms

$$\sum m(\{a\}) = \overline{\prod M(\{a\})}$$

$$\begin{aligned}\overline{\prod M(\{a\})} &= \overline{(M_{a_1} \cdot M_{a_2} \cdot \dots \cdot M_{a_k})} \\ &= \overline{M_{a_1}} + \overline{M_{a_2}} + \dots + \overline{M_{a_k}} \\ &= m_{a_1} + m_{a_2} + \dots + m_{a_k} = \sum m(\{a\})\end{aligned}$$

E.g.  $M_0' = (A+B+C)' = A'B'C' = m_0$



# Why canonical SoP and PoS?

Canonical SOP and POS are unique for each boolean function

Provides a concise and unique way of representing a truth table

We can use a specific set of rules that guarantee the simplest function for any logic expression

# Elements of Combinational Logic Design

# Outline

1. Implementing boolean logic circuits
  - a. Standard form
  - b. Canonical form
2. Simplifying logic circuits
3. Universal gates
  - a. NAND/NOR implementations

# Implementing boolean logic circuits

# Typical architecture to implement a standard form

Level 1 - to complement some of the variables ( this might be skipped in some diagrams)

Level 2 -

- AND gates for SoP
- OR gates for PoS

Level 3 -

- One n-input OR gate for SoP for getting the sum of everything
- One n-input AND gate for PoS for getting the product of everything


SoP: AND-OR implementation

PoS: OR-AND implementation

# Example of AND-OR Standard Form


$$F = A'BC + ABC' + AC$$

Standard form but not canonical

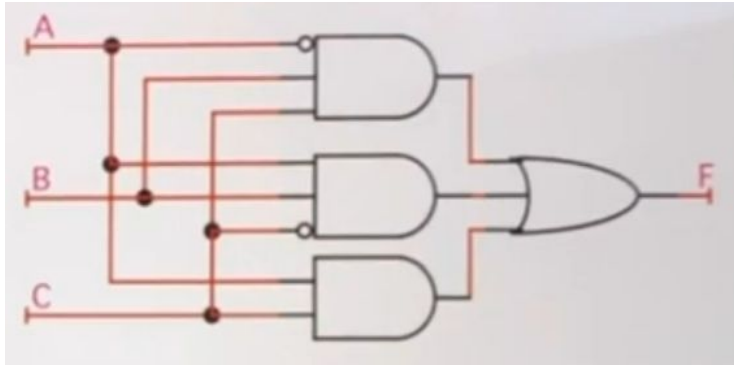

$$F = B(A'C + AC') + AC$$

(Non-standard form)

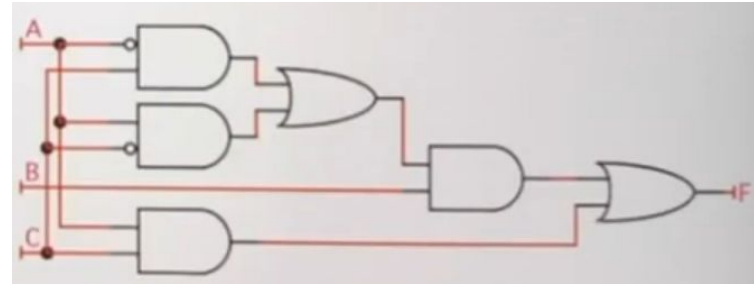

- Fewer inputs but more gate levels
- Comparison & implementation is more difficult than with the standard form


# Same example in canonical form

Sum of minterms

$$F = A'BC + ABC' + AC$$

$$= A'BC + ABC' + AC(B+B')$$

$$= A'BC + ABC' + ACB + ACB'$$

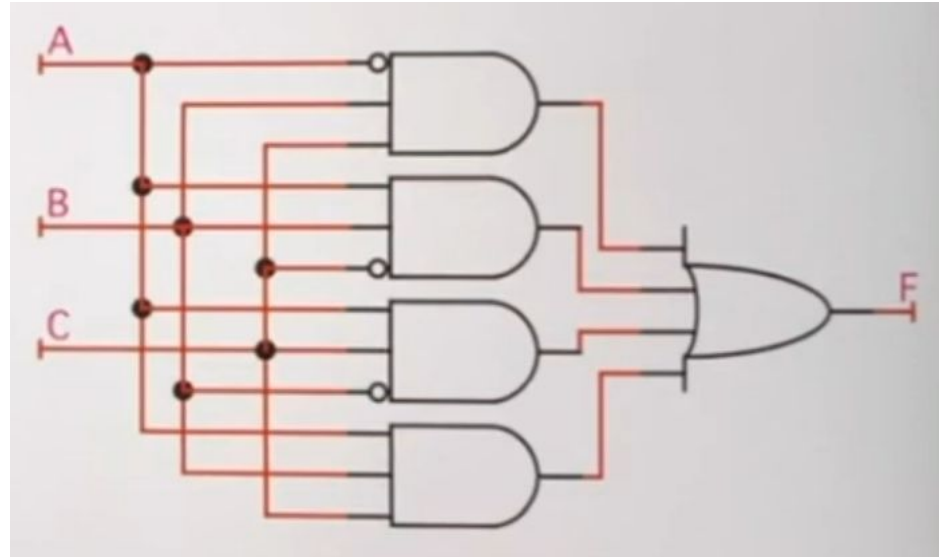

# Simplifying standard forms

- Two-level minimum cost design
  - PoS or SoP with the minimum number of terms
  - Each term has the minimum number of literals
- How to get the simplest design systematically?
  - Karnaugh maps!




# Universal Gates


# Universal gate

- A gate is a universal gate if a collection of that gates can be arranged to implement AND, OR & NOT gates
- All circuits can be represented in standard form
  - I.e. all circuits can be built with AND, OR, NOT
  - Therefore, a universal gate can be used to implement any circuit
- A universal gate is “functionally complete”

# Is NAND universal?

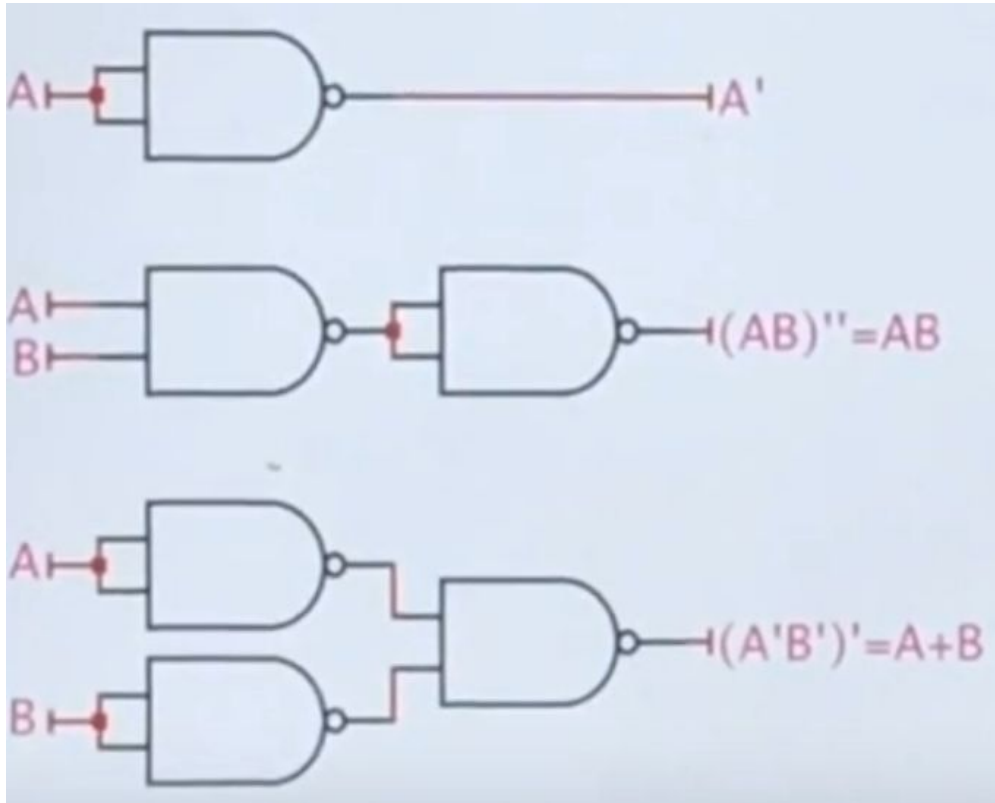

# Is NOR universal?

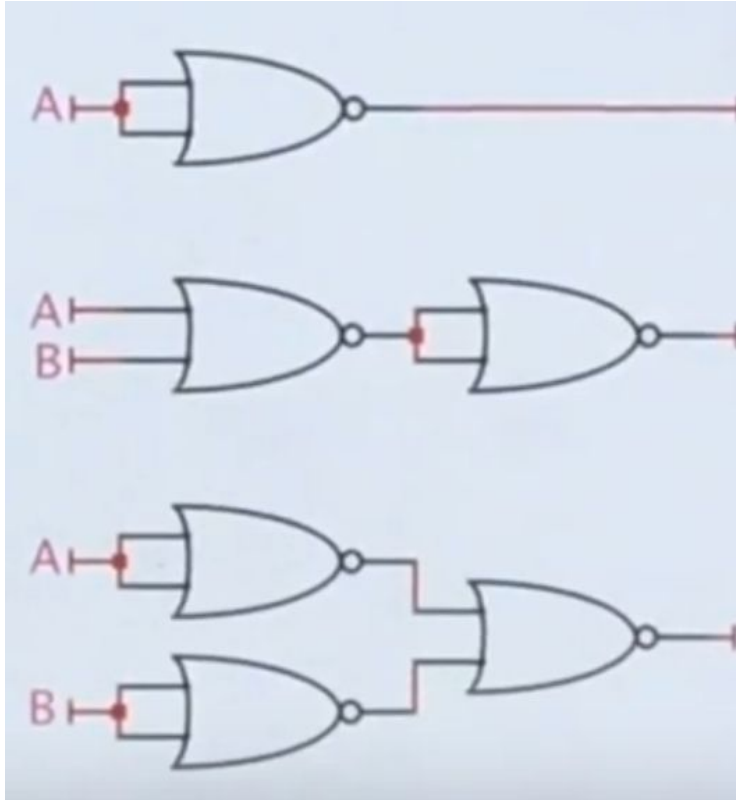

$A'$

$(A+B)'' = A+B$



$(A'+B')' = A.B$

# NAND and NOR implementation of circuits

- Function-based approach
  - Use De Morgan's law to move from AND-OR to NAND-NOR
  - E.g.  $AB+CD = (AB+CD)'' = ((AB)'(CD)')'$
- Circuit-based approach
  - Replace all gates with NAND gates
  - Undo any complements caused by the replacement

NAND & NOR gates are generally faster than AND & OR gates in most technologies
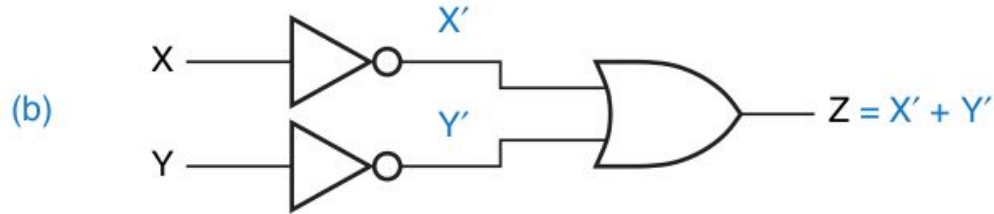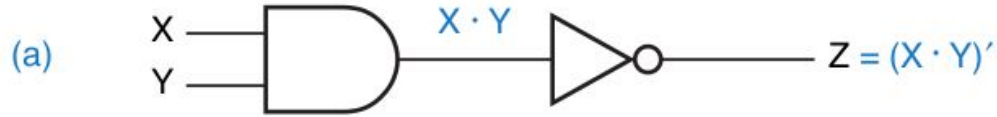
# NAND equivalent circuits (De Morgan's theorem)



# Implementation of NOR



- Note the equivalence (De Morgan's law)
  - $(A+B)' = A'.B'$
- If you take the complement of both sides, we get another equivalence
  - $A+B = (A'.B')'$  (i.e. NAND of inverted inputs)

# NOR equivalent circuits (De Morgan's theorem)


Try it out (somewhat parallel to slide 30)



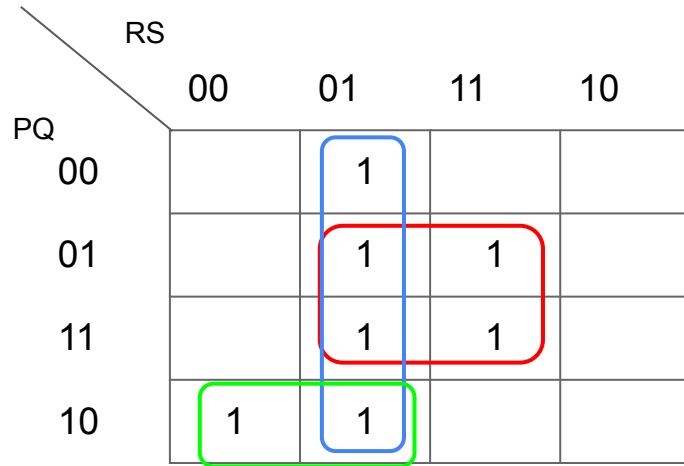
# Example

$$F = PQS + P'R'S + PQ'R' + P'QRS$$

Step 1: Simplify this using a Karnaugh Map



$$QS + R'S + PQ'R'$$

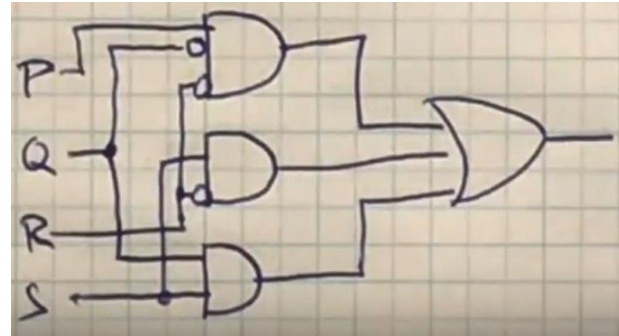

# Example

$$F = QS + R'S + PQ'R'$$

To implement this using NAND gates:


Step 2 - invert and invert again, to use De Morgan's law

$$F = F'' = (QS + R'S + PQ'R')''$$


$$= ((QS)'.(R'S)'.(PQ'R'))'$$

Homework: Draw the circuit
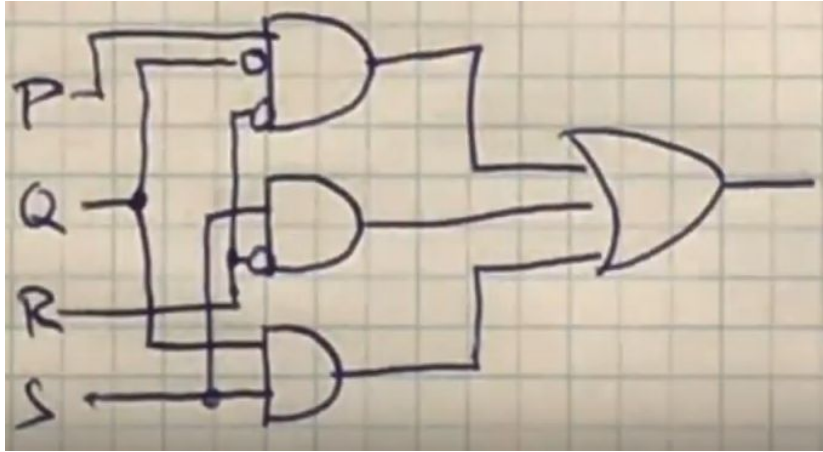
## Example: Circuit based approach to convert to NAND




$$QS + R'S + PQ'R'$$

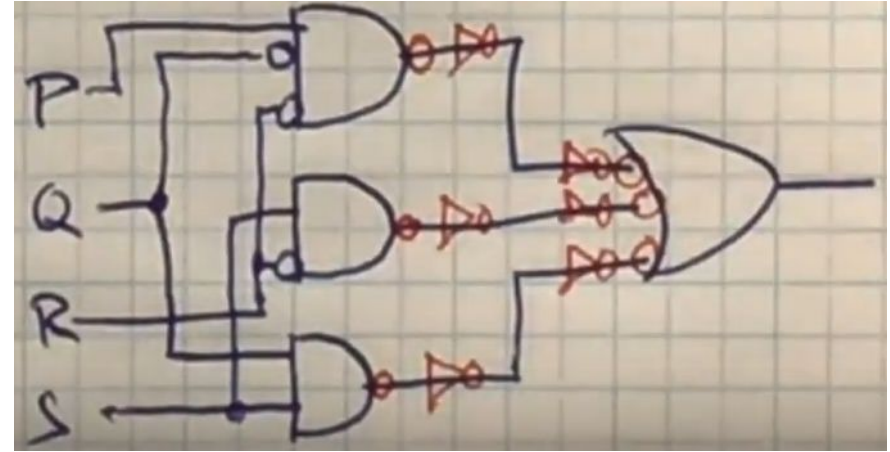

- Replace AND with NAND
  - Add NOT to fix unwanted inversions
- Convert OR into NAND by inverting the inputs (De Morgan, Slide 28)
  - Add NOTs to fix unwanted inversions
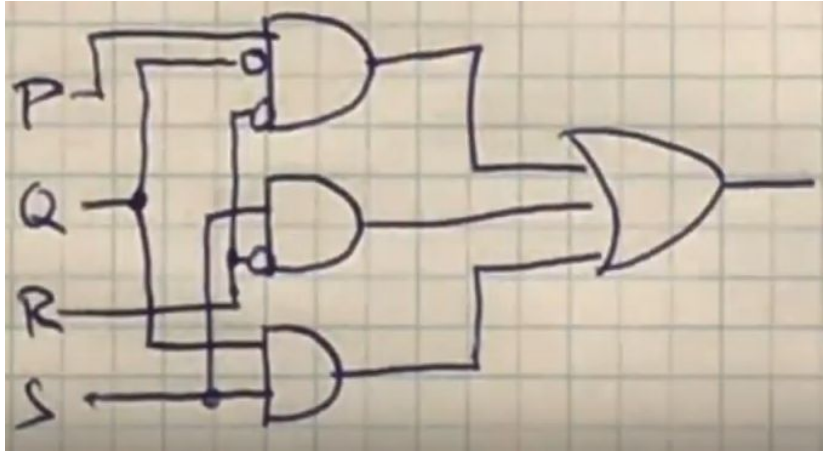
## Example: Circuit based approach to convert to NAND



$$QS + R'S + PQ'R'$$

- Simplify the NOT gates that cancel each other out

# Deriving / simplifying boolean functions: beyond K-maps

- K-maps are typically used for cases where there are 4 variables or less
- For more complex cases, particularly when multiple outputs are involved, there are other algorithms which are more suitable
  - Quine-McCluskey algorithms
    - This is a programmed minimization method
    - Typically, a high-level programming language implementation is used for running the algorithms